

Designing Oscillator for an Antenna at ~ 3.5 GHz

2896

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

Milestones completed so far

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

Topology of Ideal Transistor Circuit

Collpit's Oscillator

- The non-feedback Collpit's version was used for better performance at high frequencies
- The circuit was tested with no load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

^a

^aFull Derivation in the Appendix

Collpit's Oscillator

- The non-feedback Collpit's version was used for better performance at high frequencies
- The circuit was tested with no load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

^a

Collpit's Oscillator

- The non-feedback Collpit's version was used for better performance at high frequencies
- The circuit was tested with no load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

^a

^aFull Derivation in the Appendix

Output Waveform



Choosing the BJT

Required characteristics



Testing with Load and Choosing a Matching Network

Next Steps

Appendix

Proof of operating frequency

BFP520 Spice File

```
*$
.SUBCKT BFP520/INF 200 100 300
L1 1 10 0.47nH
L2 2 20 0.56nH
L3 3 30 0.23nH
C1 10 20 6.9fF
C2 20 30 134fF
C3 30 10 136fF
L4 10 100 0.53nH
L5 20 200 0.58nH
L6 30 300 0.05nH
Q1 2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17 NF =1 NR =1
+ ISE=2.5E-14 NE =2 ISC=2E-14
+ NC =2 BF =235 BR =1.5
+ VAF=25 VAR=2 IKF=0.4
+ IKR=0.01 RB =11 RBM=7.5
+ RE =0.6 RC =7.6 CJE=2.35E-13
+ VJE=0.958 MJE=0.335 CJC=9.3E-14
+ VJC=0.661 MJC=0.236 CJS=0
+ VJS=0.75 MJS=0.333 FC=0.5
+ XCJC=1 TF=1.7E-12 TR=5E-08
+ XTF=10 ITF=0.7 VTF=5
+ PTF=50 XTB=-0.25 XTI=0.035
+ EG=1.11)
```

*\$

Calculation of matching network

Bibliography