



# Designing Oscillator for an Antenna at $\sim 3.5$ GHz

2896

---

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

## Milestones completed so far

---

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.



## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.



# Choosing the BJT

---

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above  $3.5[GHz]$ .
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)



## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)



## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]



---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

# Data from Infenion - 1

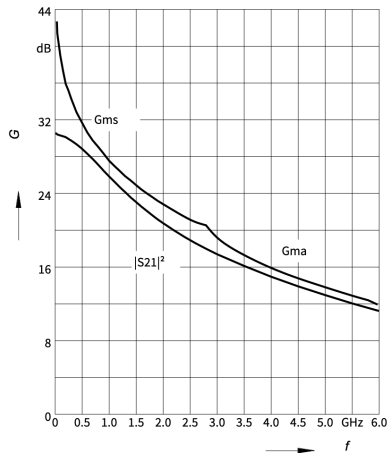 

## Data from Infenion - 2

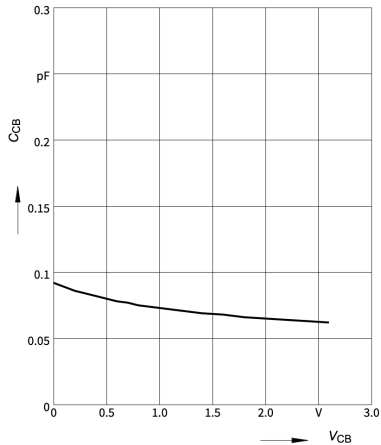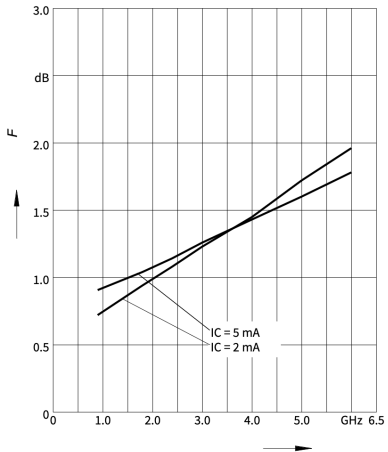



# Oscillator Circuit

---






# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

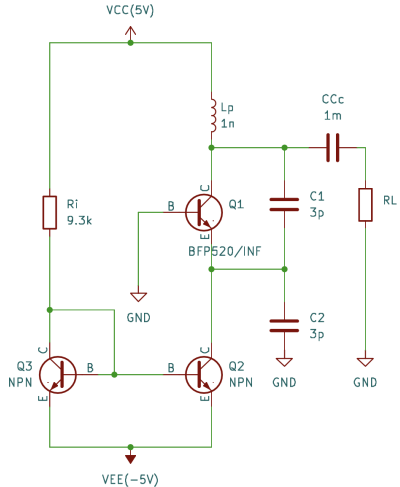- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency




# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

 - $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



## Output Waveform



# Choosing a Matching Network

---

# Why Matching Network

- The oscillator we have works for high  $R_L$ . Having low  $R_L$ , such as  $50[\Omega]$  fails to satisfy  $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts  $R_L = 50[\Omega]$  to the  $R_L$  we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.

# Why Matching Network

- The oscillator we have works for high  $R_L$ . Having low  $R_L$ , such as  $50[\Omega]$  fails to satisfy  $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts  $R_L = 50[\Omega]$  to the  $R_L$  we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.


# Why Matching Network

- The oscillator we have works for high  $R_L$ . Having low  $R_L$ , such as  $50[\Omega]$  fails to satisfy  $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts  $R_L = 50[\Omega]$  to the  $R_L$  we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.
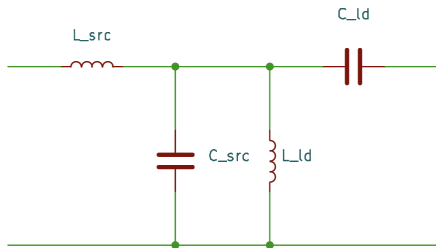
# Matching Network

The following is the matching network used<sup>2</sup>

$$\begin{cases} L_{src} = \\ C_{src} = \\ L_{ld} = \\ C_{ld} = \end{cases}$$



---

<sup>2</sup>Design method in Appendix



## S-parameters of the Matching Network

Tested with  $R_S = 1000[\Omega]$  and  $R_L = 50[\Omega]$

## Output of Oscillator using Matching Network as $50[\Omega]$ load



# Efficiency $\eta$

---

## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$ <sup>3</sup>

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$ <sup>3</sup>

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$ <sup>3</sup>

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

## Calculation of $\eta$

## Next Steps

---



## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

# Appendix

---

## Proof of operating frequency

# BFP520 Spice File

```
*$
.SUBCKT BFP520/INF 200 100 300
L1 1 10 0.47nH
L2 2 20 0.56nH
L3 3 30 0.23nH
C1 10 20 6.9fF
C2 20 30 134fF
C3 30 10 136fF
L4 10 100 0.53nH
L5 20 200 0.58nH
L6 30 300 0.05nH
Q1 2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17      NF =1          NR =1
+ ISE=2.5E-14      NE =2          ISC=2E-14
+ NC =2            BF =235        BR =1.5
+ VAF=25           VAR=2          IKF=0.4
+ IKR=0.01         RB =11         RBM=7.5
+ RE =0.6          RC =7.6        CJE=2.35E-13
+ VJE=0.958        MJE=0.335      CJC=9.3E-14
+ VJC=0.661        MJC=0.236      CJS=0
+ VJS=0.75         MJS=0.333      FC=0.5
+ XCJC=1           TF=1.7E-12     TR=5E-08
+ XTF=10           ITF=0.7        VTF=5
+ PTF=50           XTB=-0.25      XTI=0.035
+ EG=1.11)

```

\*\*\*\*\*

\*\$

## Calculation of matching network