

Designing Oscillator for an Antenna at $\sim 3.5[GHz]$

2896

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

Milestones completed so far

List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency

List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency

List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency

List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency



Choosing the BJT

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

BFP520 from Infenion¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infenion¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infenion¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infenion¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infineon¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a



Oscillator Circuit


Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

a

 - $C_1 = C_2$ was chosen since it gave the highest oscillation frequency



^aIn-depth analysis in Appendix


Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

a

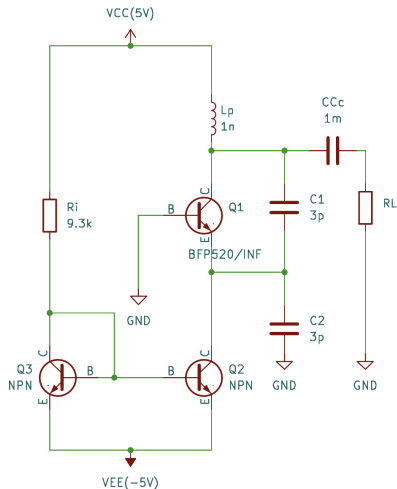- $C_1 = C_2$ was chosen since it gave the highest oscillation frequency



^aIn-depth analysis in Appendix


Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

a

 - $C_1 = C_2$ was chosen since it gave the highest oscillation frequency



^aIn-depth analysis in Appendix


Output Waveform

Choosing a Matching Network

Matching Network





T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.²

 - $L_{src} = 2.03361[nH]$
- $C_{src} = 2.02955[fF]$
- $L_{ld} = 10.4421[nH]$
- $C_{ld} = 0.208424[pF]$



²Design method in Appendix


S-parameters of the Matching Network³

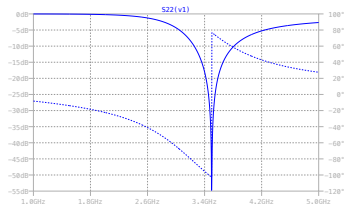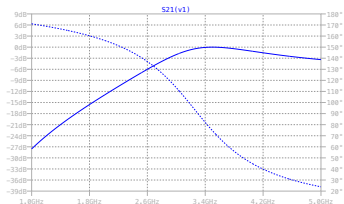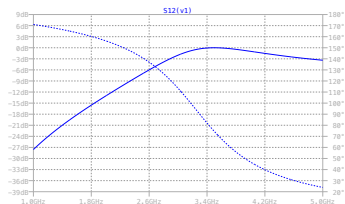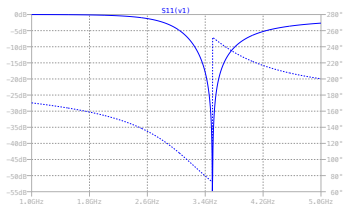

³Simulated using .net parameter in LTSpice


Input impedance through the Matching Network

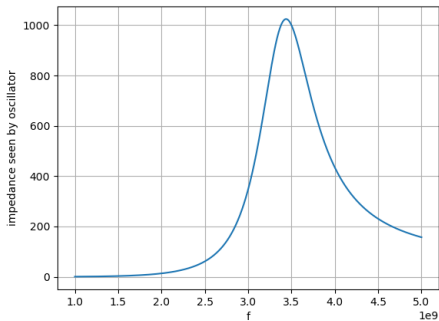- Attains max value of $\approx 1000[\Omega]$ at $3.5[GHz]$
- Tapers quickly for the non-central frequencies



Oscillator using Matching Network as $50[\Omega]$ load

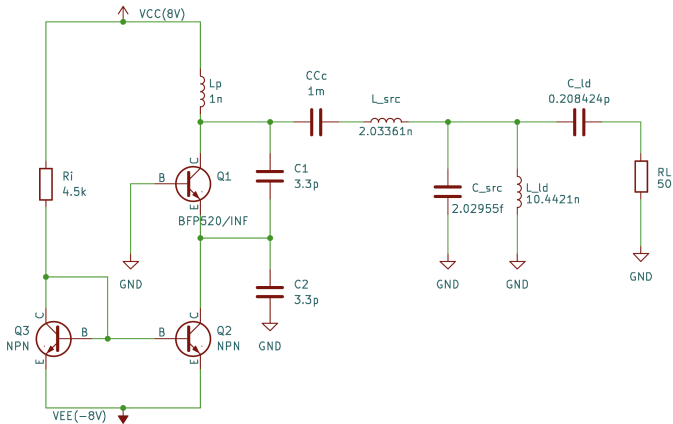After making adjustments to supply and current to maximise efficiency, we have the following system⁴



⁴Efficiency η is defined in the next section

Output of Oscillator using Matching Network as $50[\Omega]$ load



Efficiency η

Calculation of η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$

Calculation of η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$

Calculation of η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$

Calculation of η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$

For $V_{CC} = -V_{EE} = 8[V]$, and current mirror set to give $3.36[mA]$, we have $v_p = 1.6[V]$, giving us

$$\eta \approx 20\%^5$$

⁵It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%, implying we have a decent efficiency

Antenna Design

Patch Microstrip Antenna



Next Steps

Next Steps



- Layout the PCB
- Fabrication and Testing

Next Steps



- Layout the PCB
- Fabrication and Testing

Appendix

Data from Infenion - 1

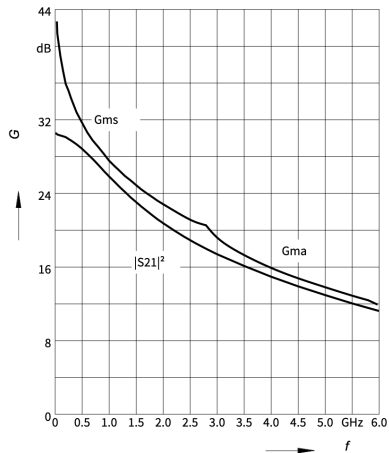 

Data from Infenion - 2

  


BFP520 Spice File

```
*$
.SUBCKT BFP520/INF 200 100 300
L1    1    10    0.47nH
L2    2    20    0.56nH
L3    3    30    0.23nH
C1    10   20    6.9fF
C2    20   30    134fF
C3    30   10    136fF
L4    10   100   0.53nH
L5    20   200   0.58nH
L6    30   300   0.05nH
Q1    2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17      NF =1          NR =1
+ ISE=2.5E-14      NE =2          ISC=2E-14
+ NC =2            BF =235        BR =1.5
+ VAF=25           VAR=2          IKF=0.4
+ IKR=0.01         RB =11         RBM=7.5
+ RE =0.6          RC =7.6        CJE=2.35E-13
+ VJE=0.958        MJE=0.335      CJC=9.3E-14
+ VJC=0.661        MJC=0.236      CJS=0
+ VJS=0.75         MJS=0.333      FC=0.5
+ XCJC=1           TF=1.7E-12     TR=5E-08
+ XTF=10           ITF=0.7        VTF=5
+ PTF=50           XTB=-0.25      XTI=0.035
+ EG=1.11)
*****
```

*\$

Proof of operating frequency - 1

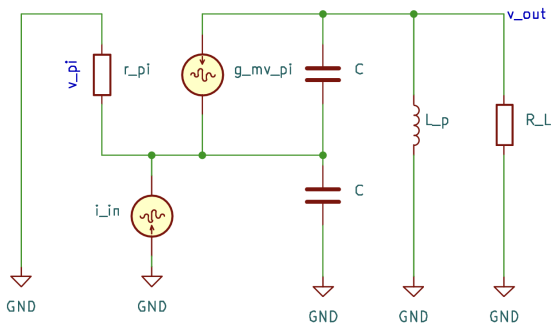We have the following small signal model of Collpit's oscillator, with $C_1 = C_2 = C$ ⁶



⁶In all the results, we try to ignore effects of r_{π} and then adjust the values accordingly to get required response

Proof of operating frequency - 2

$$i_{in} = -\frac{v_{\pi}}{r_{\pi}} - sC(v_{out} + 2v_{\pi})$$

$$g_m v_{\pi} + sC(v_{out} + v_{\pi}) + \frac{v_{out}}{sL_p} + \frac{v_{out}}{R_L} = 0$$

This gives us the following frequency response

$$\frac{v_{out}}{i_{in}} = \frac{r_{\pi} L_p R_L (s^2 C + s g_m)}{r_{\pi} C^2 L_p R_L s^3 + (-r_{\pi} C L_p R_L g_m + 2r_{\pi} C L_p + C L_p R_L) s^2 + (2r_{\pi} C R_L + L_p) s + R_L}$$

Put $s = j\omega$ and let Im of denominator $\rightarrow 0$

$$\omega_0 = \sqrt{\frac{2r_{\pi} C R_L + L_p}{r_{\pi} C^2 L_p R_L}}$$

Assuming $r_{\pi} \rightarrow \infty$, as is the case is MOS, we reach the well-known expression $\omega_0 = \sqrt{\frac{1}{L \frac{C \cdot C}{C+C}}}$

Proof of operating frequency - 3

For sustained oscillations, we need

$$-(-r_{\pi}CL_pR_Lg_m + 2r_{\pi}CL_p + CL_pR_L)\omega_0^2 + R_L > 0$$

This gives us

$$^7R_Lg_m - \frac{R_L}{r_{\pi}} - 2 > 0$$

Thus, we need to set R_L accordingly at the oscillating frequency, giving us a lower bound for load and thus a need for a matching network

⁷This is similar to the condition found in Razavi, but for NMOS in place of NPN BJT

Calculation of matching network - 1

We have a source impedance Z_s , a load impedance Z_L , and operating frequency f_0 and we need to match Z_L to Z_s at f_0 using a T-Matching Network. We assume a central impedance Z_c such that $Z_c > \max(Z_s, Z_L)$, and then calculate the series and parallel reactive components on both sides.⁸

Source:

$$Q_{src} = \sqrt{\frac{Z_c}{Z_s} - 1}$$

$$X_{src}^{parallel} = \frac{Z_c}{Q_{src}}$$

$$X_{src}^{series} = Q_{src} Z_s$$

Load:

$$Q_{ld} = \sqrt{\frac{Z_c}{Z_L} - 1}$$

$$X_{ld}^{parallel} = \frac{Z_c}{Q_{ld}}$$

$$X_{ls}^{series} = Q_{ls} Z_L$$

Then, $L = \frac{X}{2\pi f_0}$ and $C = \frac{1}{2\pi f_0 X}$ for chosen X series/parallel

⁸In our case, all impedances are real





Calculation of matching network - 2⁹



After this, the values of V_{cc} , V_{ee} , and I_c were changed so as to get the max efficiency. R_L was matched to $1[K\Omega]$.

Variable	Value
f_0	3.5×10^9
Z_{out_osc}	1000
Z_{load}	50
Z_{center}	1002
Q_{src}	0.0447214
$X_{paralle_src}$	22405.4
X_{series_src}	44.7214
L_{src}	2.03361×10^{-9}

Variable	Value
C_{src}	2.02955×10^{-15}
Q_{ld}	4.36348
$X_{paralle_ld}$	229.633
X_{series_ld}	218.174
L_{ld}	1.04421×10^{-8}
C_{ld}	2.08424×10^{-13}
C_{com}	2.10454×10^{-13}
L_{com}	1.70212×10^{-9}

⁹Values generated using .py script that we made

-  T. K. Johnson, “A colpitts oscillator design technique using s-parameters,” 1986.
-  X. Li, S. Shekhar, and D. Allstot, “G/sub m/-boosted common-gate lna and differential colpitts vco/qvco in 0.18-/spl mu/m cmos,” *Solid-State Circuits, IEEE Journal of*, vol. 40, pp. 2609 – 2619, 01 2006.
-  D. M. Pozar, *Microwave engineering; 3rd ed.*
Hoboken, NJ: Wiley, 2005.
-  B. Razavi, *Design of Analog CMOS Integrated Circuits.*
McGraw-Hill, first ed., 2001.

-  F. Ullah, Y. Liu, Z. Li, X. Wang, M. Sarfraz, and H. Zhang, “A bandwidth-enhanced differential lc-voltage controlled oscillator (lc-vco) and superharmonic coupled quadrature vco for k-band applications,” *Electronics*, vol. 7, p. 127, 07 2018.
-  M. Giuseppe, *Comparison of Voltage-Controlled-Oscillator Architectures for Implementation in 180 nm SiGe Technology*.
PhD thesis, 12 2016.