

Designing Oscillator for an Antenna at ~ 3.5 GHz

2896

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

Milestones completed so far

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}

List of Milestones completed

- Created test schematic for oscillator using an ideal transistor
- Ran LTSpice Simulations for the ideal version
- Selected an RF transistor with a required performance at the interested frequency
- Ran PSpice Simulations for the same schematic but with non-ideal transistor
- Collected useful data like S-parameters, Z-parameters, Z_{in} and Z_{out} in order to build matching network
- Built matching network for Z_{out} and $Z_{load} = 50[\Omega]$ at $\sim 3.5[GHz]$
- Tested the power output of the circuit for the matching and adjusted the values to maximize power transfer between the DC sources and Z_{load}



Choosing the BJT

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above $3.5[GHz]$.
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above $3.5[GHz]$.
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

Required characteristics

- The transistor needs high-frequency performance, including f_{\max} and f_t , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

BFP520 from Infineon¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infineon¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infineon¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infineon¹

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]



¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

BFP520 from Infineon¹



- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency f_T of 45[GHz]
- High Gain, with $|S_{12}|$, G_{ma} , $G_{ms} > 16[dB]$ at 3.5[GHz] under $V_{ce} = 2[V]$
- Low Noise Figure, $NF < 1.2[dB]$ at 3.5[GHz], 2[V], 2[mA]

¹https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a

Data from Infenion - 1

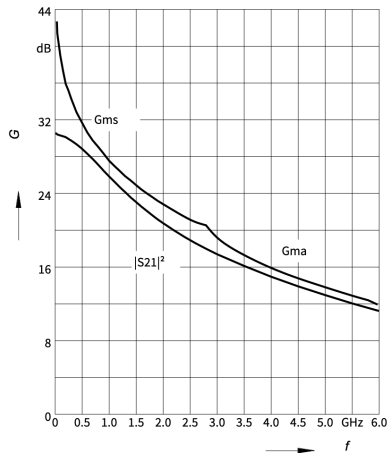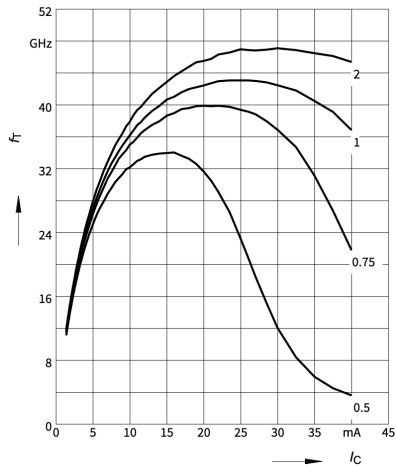

Data from Infenion - 2

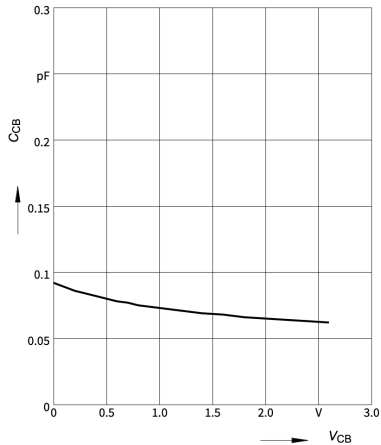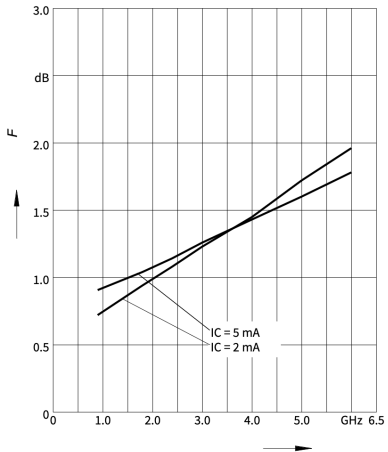




Oscillator Circuit

Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

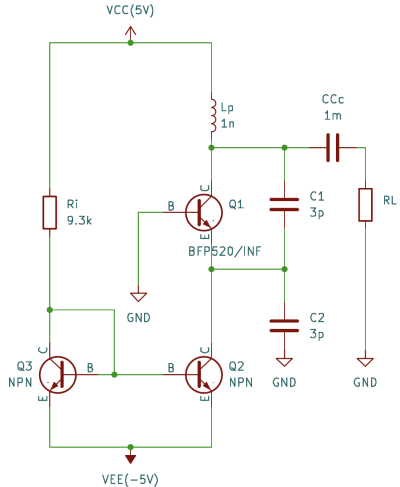- $C_1 = C_2$ was chosen since it gave the highest oscillation frequency




Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

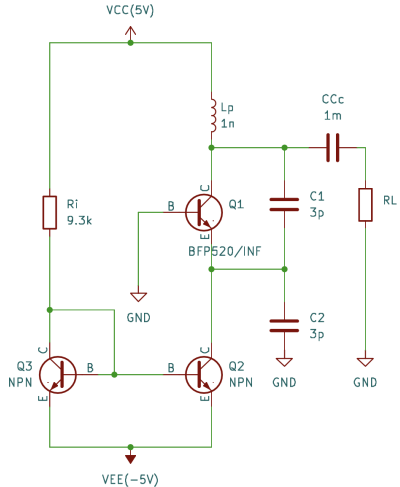- $C_1 = C_2$ was chosen since it gave the highest oscillation frequency




Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of L_p , C_1 and C_2 were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi\sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

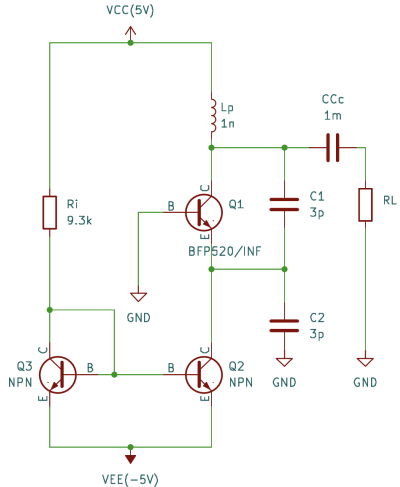- $C_1 = C_2$ was chosen since it gave the highest oscillation frequency



Output Waveform



Choosing a Matching Network

Why Matching Network

- The oscillator we have works for high R_L . Having low R_L , such as $50[\Omega]$ fails to satisfy $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts $R_L = 50[\Omega]$ to the R_L we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.

Why Matching Network

- The oscillator we have works for high R_L . Having low R_L , such as $50[\Omega]$ fails to satisfy $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts $R_L = 50[\Omega]$ to the R_L we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.


Why Matching Network

- The oscillator we have works for high R_L . Having low R_L , such as $50[\Omega]$ fails to satisfy $g_m R_L^{eff} \gg 4$
- We need to design a matching network that converts $R_L = 50[\Omega]$ to the R_L we have in the schematic
- We used a T-Matching network. T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.

Matching Network

The following is the matching network used²
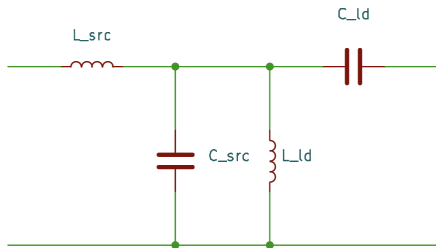
$$\begin{cases} L_{src} = \\ C_{src} = \\ L_{ld} = \\ C_{ld} = \end{cases}$$



²Design method in Appendix

S-parameters of the Matching Network

Tested with $R_S = 1000[\Omega]$ and $R_L = 50[\Omega]$

Output of Oscillator using Matching Network as $50[\Omega]$ load



Efficiency η

Defining η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$ ³

³It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

Defining η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$ ³

³It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

Defining η

- **Input:** $P_{DC} = V_{CC}I_C$
- **Output:** $P_{ac} = \frac{V_{rms}^2}{R_L}$ where $V_{rms} = \frac{V_{max}}{\sqrt{2}}$ for the output waveform
- **Efficiency:** $\eta = \frac{P_{ac}}{P_{CD}}$ ³

³It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

Calculation of η

Next Steps

Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

Appendix

Proof of operating frequency

BFP520 Spice File

```
*$
.SUBCKT BFP520/INF 200 100 300
L1 1 10 0.47nH
L2 2 20 0.56nH
L3 3 30 0.23nH
C1 10 20 6.9fF
C2 20 30 134fF
C3 30 10 136fF
L4 10 100 0.53nH
L5 20 200 0.58nH
L6 30 300 0.05nH
Q1 2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17      NF =1          NR =1
+ ISE=2.5E-14      NE =2          ISC=2E-14
+ NC =2            BF =235        BR =1.5
+ VAF=25           VAR=2          IKF=0.4
+ IKR=0.01         RB =11         RBM=7.5
+ RE =0.6          RC =7.6        CJE=2.35E-13
+ VJE=0.958        MJE=0.335      CJC=9.3E-14
+ VJC=0.661        MJC=0.236      CJS=0
+ VJS=0.75         MJS=0.333      FC=0.5
+ XCJC=1           TF=1.7E-12     TR=5E-08
+ XTF=10           ITF=0.7        VTF=5
+ PTF=50           XTB=-0.25      XTI=0.035
+ EG=1.11)

```

*\$

Calculation of matching network