

# Designing Oscillator for an Antenna at $\sim 3.5[GHz]$

2896

---

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

Milestones completed so far

---

## List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency
- Designed Antenna

## List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency
- Designed Antenna

# List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency
- Designed Antenna

## List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency
- Designed Antenna

## List of Milestones completed

- Selected the transistor we will use
- Simulated the oscillator we designed in PSpice
- Designed Matching network for the load(antenna)
- Optimised matching network for efficiency
- Designed Antenna

## Choosing the BJT

---



## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## BFP520 from Infenion<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## **BFP520** from Infenion<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## **BFP520** from Infenion<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)



## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## **BFP520** from Infenion<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

# Oscillator Circuit

---


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

*a*

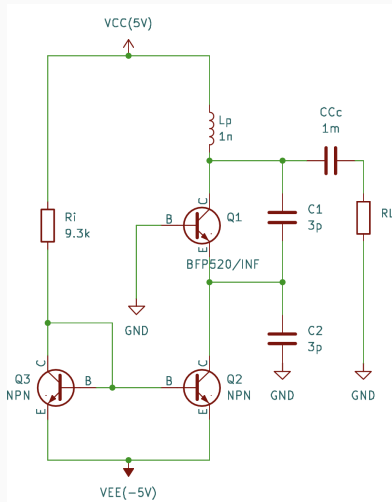- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

*a*

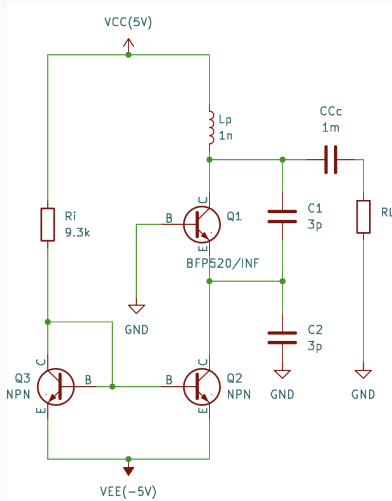- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

*a*

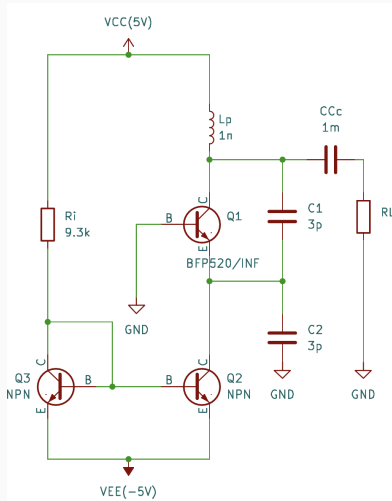- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix


# Choosing a Matching Network

---
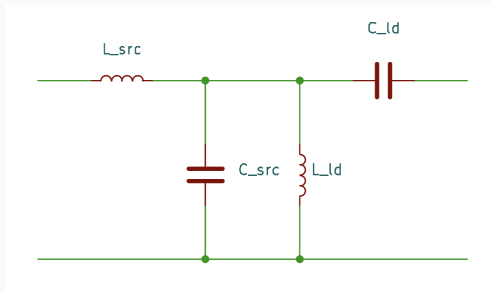
# Matching Network

For oscillation to function, we need at-least  $R_L \approx 1[k\Omega]$ . Thus, we need to match  $50[\Omega] \rightarrow 1[k\Omega]$  at  $3.5[GHz]$ . T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.<sup>2</sup>

- $L_{src} = 2.03361[nH]$
- $C_{src} = 2.02955[fF]$
- $L_{ld} = 10.4421[nH]$
- $C_{ld} = 0.208424[pF]$







---

<sup>2</sup>Design method in Appendix



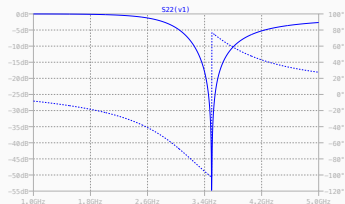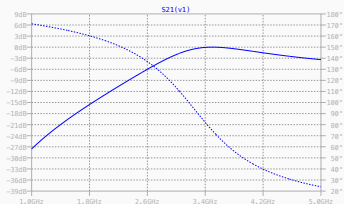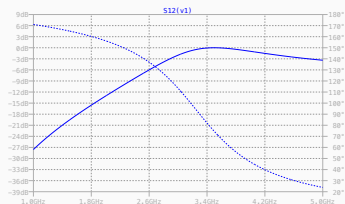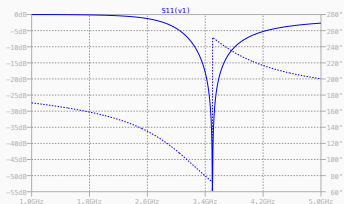
# S-parameters of the Matching Network<sup>3</sup>



<sup>3</sup>Simulated using .net parameter in LTSpice

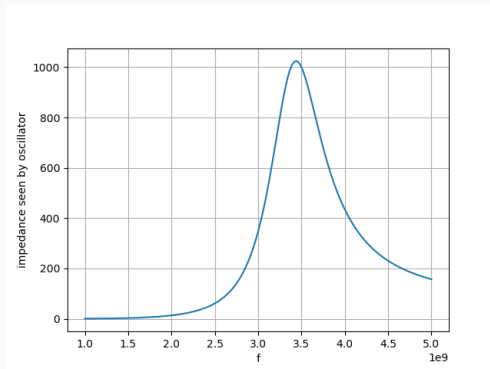
# Input impedance through the Matching Network

- Attains max value of  $\approx 1000[\Omega]$  at  $3.5[GHz]$
- Tapers quickly for the non-central frequencies


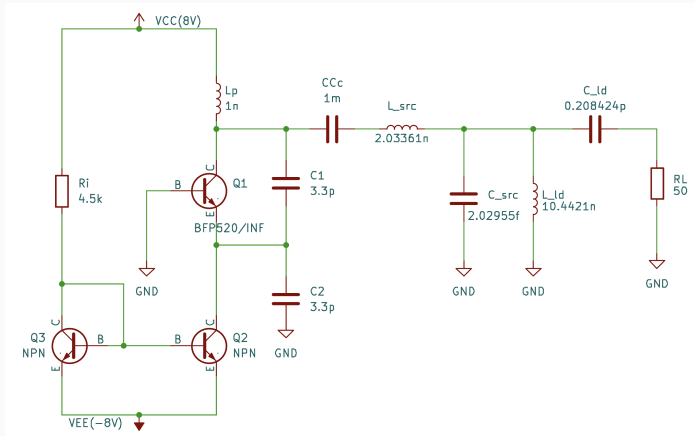
# Oscillator Simulation


After making adjustments to supply and current to maximize efficiency, we have the following system<sup>4</sup>



<sup>4</sup>Efficiency  $\eta$  is defined in the next section
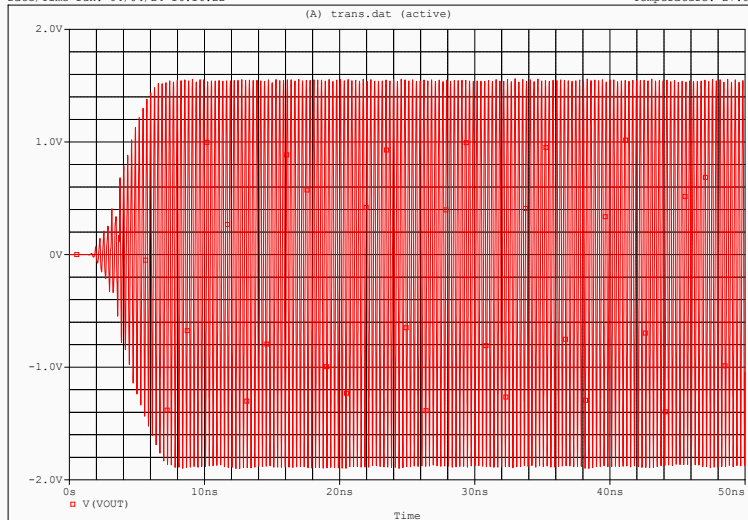
# Output of Oscillator - Transient

\*\* Profile: "SCHEMATIC1-trans" [ \\mac\home\university-projects\vco-transmitter\oscillator\update-oscil...  
Date/Time run: 04/04/24 16:16:22 Temperature: 27.0




Date: April 04, 2024

Page 1

Time: 16:17:10
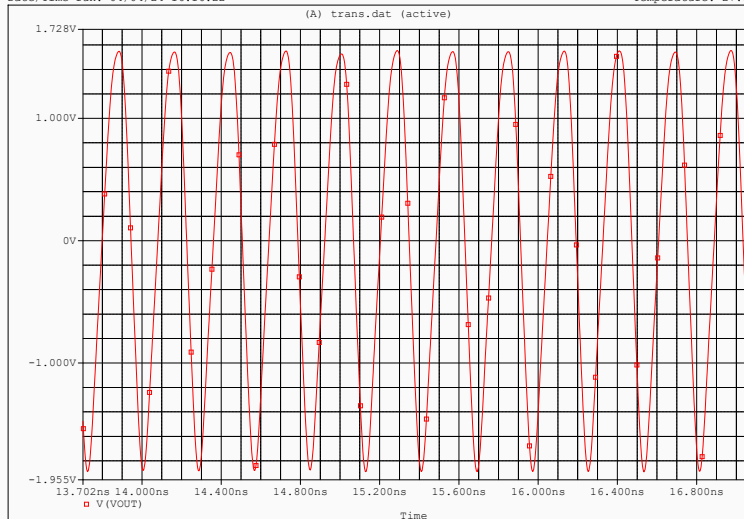
# Output of Oscillator - Transient Zoomed

\*\* Profile: "SCHEMATIC1-trans" [ \\mac\home\university-projects\vco-transmitter\oscillator\update-oscil...  
Date/Time run: 04/04/24 16:16:22 Temperature: 27.0




Date: April 04, 2024

Page 1

Time: 16:17:37
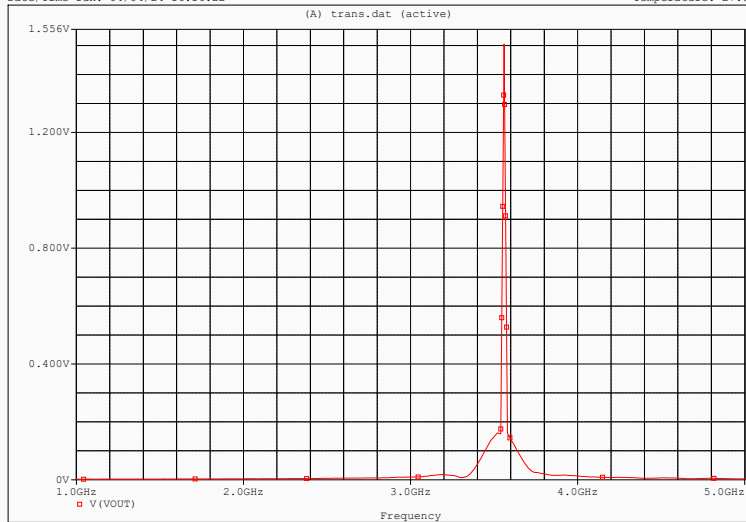
# Output of Oscillator - Fast Fourier Transform

\*\* Profile: "SCHEMATIC1-trans" [ \\mac\home\university-projects\vco-transmitter\oscillator\update-oscil...  
Date/Time run: 04/04/24 16:16:22 Temperature: 27.0



Date: April 04, 2024

Page 1

Time: 16:18:07

# Efficiency

---

## Calculation of $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$

---

<sup>5</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%, implying we have a decent efficiency



## Calculation of $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$

For  $V_{CC} = -V_{EE} = 8[V]$ , and current mirror set to give  $3.36[mA]$ , we have  $v_p = 1.6[V]$ , giving us

$$\eta \approx 20\%^5$$

---


<sup>5</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%, implying we have a decent efficiency

# Antenna Design

---

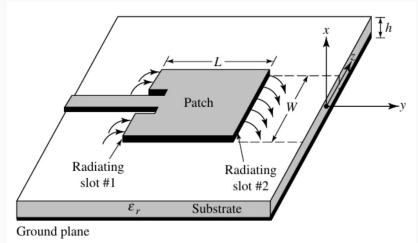
# Antenna Decisions

- Microstrip patch antenna with an inline microstrip line feed
- Input impedance of  $50[\Omega]$
- Directional Antenna with good efficiency and high gain when used in an antenna array



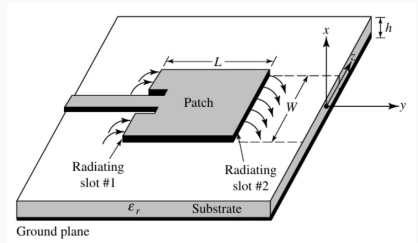
# Antenna Decisions

- Microstrip patch antenna with an inline microstrip line feed
- Input impedance of  $50[\Omega]$
- Directional Antenna with good efficiency and high gain when used in an antenna array


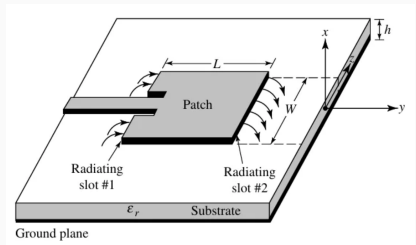
# Antenna Decisions

- Microstrip patch antenna with an inline microstrip line feed
- Input impedance of  $50[\Omega]$
- Directional Antenna with good efficiency and high gain when used in an antenna array



# Single Patch Antenna

The following antenna was used, with Rogers substrate<sup>6</sup>

| Parameter  | Value[mm] |
|------------|-----------|
| H          | 1.52      |
| W          | 28.08     |
| L          | 21.69     |
| $y_0$      | 7.89      |
| $W_{gnd}$  | 51.65     |
| $L_{gnd}$  | 45.26     |
| $W_{feed}$ | 4.70      |


---

<sup>6</sup>All the measurements are in accordance with JLCPCB guidelines - <https://jlcpcb.com/capabilities/pcb-capabilities>

# Single Patch Antenna Simulation - S parameters

CST Studio Suite 2022


1D Results\S-Parameters\S1,1

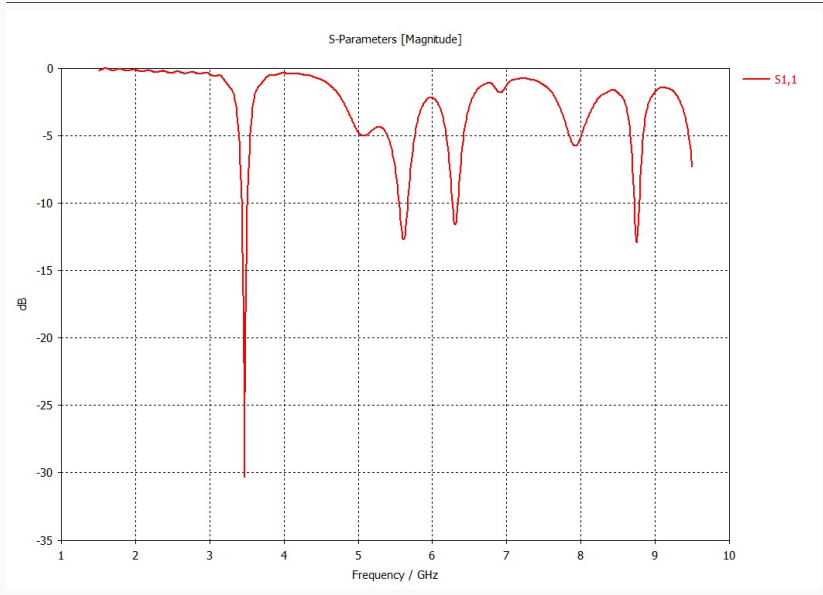

# Single Patch Antenna Simulation - Far-field

CST Studio Suite 2022

Farfields/farfield (f=3.5) [1]

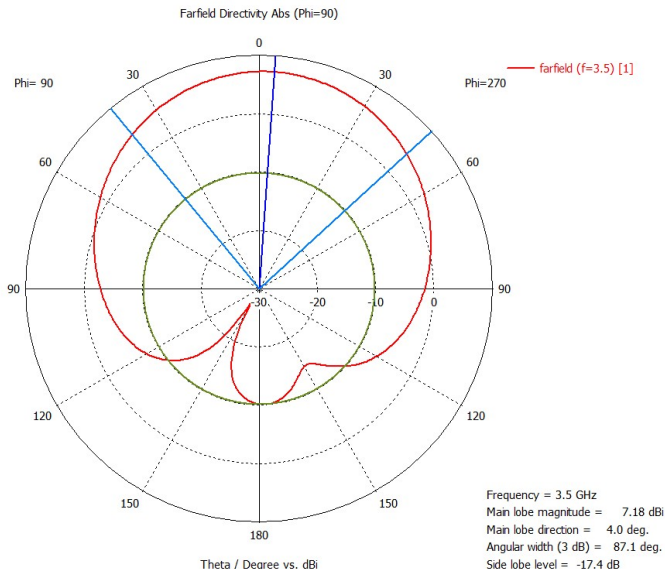



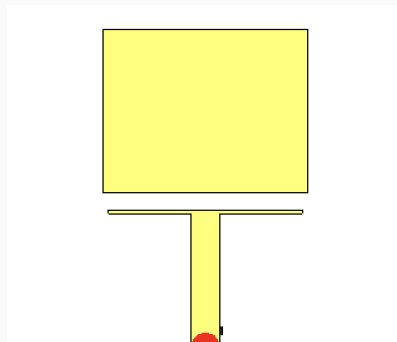
## Wideband Patch Antenna (Ongoing)

The patch antenna designed above cannot provide us the required bandwidth. Thus, the following antenna design used[?]

- Extra quarter wavelength resonators for dual resonant frequencies
- If the resonances are close enough, they can be combined to give a larger bandwidth
- Suppression of extra harmonics



# Wideband Patch Antenna Simulation - S parameters

# Wideband Patch Antenna Simulation - Far-field

## Next Steps

---

## Next Steps

- Look further into the bandwidth of the antenna
- Layout the PCB using Altium
- Fabrication and Testing

## Next Steps

- Look further into the bandwidth of the antenna
- Layout the PCB using Altium
- Fabrication and Testing

## Next Steps



- Look further into the bandwidth of the antenna
- Layout the PCB using Altium
- Fabrication and Testing

# Appendix



---



# Data from Infenion - 1

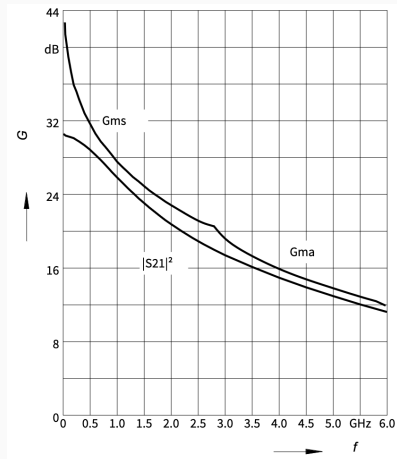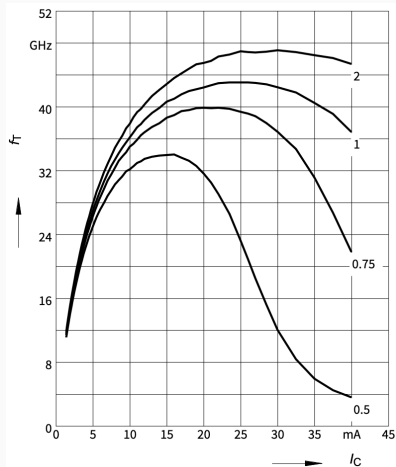

## Data from Infenion - 2

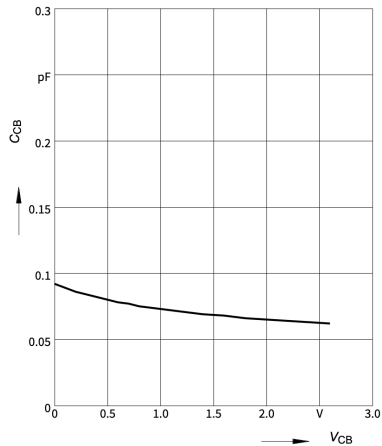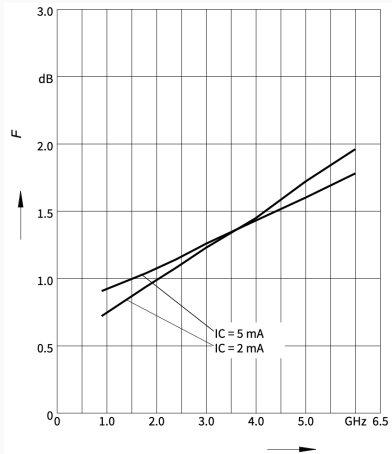


# BFP520 Spice File

```
.SUBCKT BFP520/INF 200 100 300
L1      1      10      0.47nH
L2      2      20      0.56nH
L3      3      30      0.23nH
C1      10     20      6.9fF
C2      20     30      134fF
C3      30     10      136fF
L4      10     100     0.53nH
L5      20     200     0.58nH
L6      30     300     0.05nH
Q1      2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17      NF =1      NR =1
+ ISE=2.5E-14      NE =2      ISC=2E-14
+ NC =2            BF =235    BR =1.5
+ VAF=25           VAR=2      IKF=0.4
+ IKR=0.01         RB =11     RBM=7.5
+ RE =0.6          RC =7.6    CJE=2.35E-13
+ VJE=0.958        MJE=0.335  CJC=9.3E-14
+ VJC=0.661        MJC=0.236  CJS=0
+ VJS=0.75         MJS=0.333  FC=0.5
+ XCJC=1           TF=1.7E-12 TR=5E-08
+ XTF=10           ITF=0.7    VTF=5
+ PTF=50           XTB=-0.25  XTI=0.035
+ EG=1.11)
```
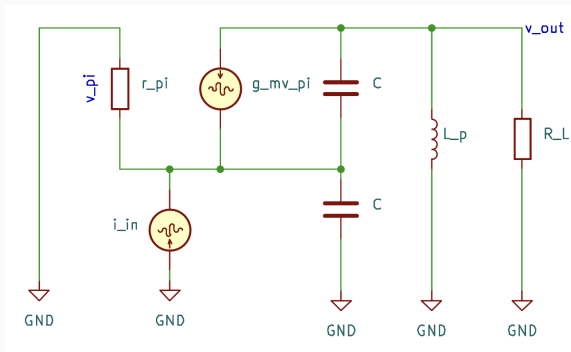
# Proof of operating frequency - 1

We have the following small signal model of Collpit's oscillator, with  $C_1 = C_2 = C^7$



---

<sup>7</sup>In all the results, we try to ignore effects of  $r_{\pi}$  and then adjust the values accordingly to get required response

## Proof of operating frequency - 2

$$i_{in} = -\frac{v_{\pi}}{r_{\pi}} - sC(v_{out} + 2v_{\pi})$$

$$g_m v_{\pi} + sC(v_{out} + v_{\pi}) + \frac{v_{out}}{sL_p} + \frac{v_{out}}{R_L} = 0$$

This gives us the following frequency response

$$\frac{v_{out}}{i_{in}} = \frac{r_{\pi} L_p R_L (s^2 C + s g_m)}{r_{\pi} C^2 L_p R_L s^3 + (-r_{\pi} C L_p R_L g_m + 2r_{\pi} C L_p + C L_p R_L) s^2 + (2r_{\pi} C R_L + L_p) s + R_L}$$

Put  $s = j\omega$  and let  $Im$  of denominator  $\rightarrow 0$

$$\omega_0 = \sqrt{\frac{2r_{\pi} C R_L + L_p}{r_{\pi} C^2 L_p R_L}}$$

Assuming  $r_{\pi} \rightarrow \infty$ , as is the case is MOS, we reach the well-known expression  $\omega_0 = \sqrt{\frac{1}{L \frac{C \cdot C}{C+C}}}$

## Proof of operating frequency - 3

For sustained oscillations, we need

$$-(-r_\pi CL_p R_L g_m + 2r_\pi CL_p + CL_p R_L)\omega_0^2 + R_L > 0$$

This gives us

$$^8 R_L g_m - \frac{R_L}{r_\pi} - 2 > 0$$

Thus, we need to set  $R_L$  accordingly at the oscillating frequency, giving us a lower bound for load and thus a need for a matching network

---

<sup>8</sup>This is similar to the condition found in Razavi, but for NMOS in place of NPN BJT

# Calculation of matching network - 1

We assume a central impedance  $Z_c$  such that  $Z_c > \max(Z_s, Z_L)$ , and then calculate the series and parallel reactive components on both sides.<sup>9</sup>

**Source:**

$$Q_{src} = \sqrt{\frac{Z_c}{Z_s} - 1}$$

$$X_{src}^{parallel} = \frac{Z_c}{Q_{src}}$$

$$X_{src}^{series} = Q_{src} Z_s$$

**Load:**

$$Q_{ld} = \sqrt{\frac{Z_c}{Z_L} - 1}$$

$$X_{ld}^{parallel} = \frac{Z_c}{Q_{ld}}$$

$$X_{ld}^{series} = Q_{ld} Z_L$$

Then,  $L = \frac{X}{2\pi f_0}$  and  $C = \frac{1}{2\pi f_0 X}$  for chosen  $X$  series/parallel

---

<sup>9</sup>In our case, all impedances are real

## Calculation of matching network - 2<sup>10</sup>

After this, the values of  $V_{cc}$ ,  $V_{ee}$ , and  $I_c$  were changed so as to get the maximum efficiency.  $R_L$  was matched to  $1[K\Omega]$ .

| Variable           | Value                    |
|--------------------|--------------------------|
| $f_0$              | $3.5 \times 10^9$        |
| $Z_{out\_osc}$     | 1000                     |
| $Z_{load}$         | 50                       |
| $Z_{center}$       | 1002                     |
| $Q_{src}$          | 0.0447214                |
| $X_{paralle\_src}$ | 22405.4                  |
| $X_{series\_src}$  | 44.7214                  |
| $L_{src}$          | $2.03361 \times 10^{-9}$ |

| Variable          | Value                     |
|-------------------|---------------------------|
| $C_{src}$         | $2.02955 \times 10^{-15}$ |
| $Q_{ld}$          | 4.36348                   |
| $X_{paralle\_ld}$ | 229.633                   |
| $X_{series\_ld}$  | 218.174                   |
| $L_{ld}$          | $1.04421 \times 10^{-8}$  |
| $C_{ld}$          | $2.08424 \times 10^{-13}$ |
| $C_{com}$         | $2.10454 \times 10^{-13}$ |
| $L_{com}$         | $1.70212 \times 10^{-9}$  |

---

<sup>10</sup>Values generated using Python script



## Parameters of a Microstrip line for required $Z_0$ [?]

For  $\frac{W}{d} \geq 1$ , we have

$$Z_0 = \frac{120\pi}{\sqrt{\epsilon_{eff}}} \frac{1}{\sqrt{\frac{W}{d} + 1.393 + 0.667 \ln \left( \frac{W}{d} + 1.444 \right)}}$$

**Solution:**

For  $W/d < 2$

$$\frac{W}{d} = \frac{8e^A}{e^{2A} - 2}$$

For  $W/d > 2$

$$\frac{W}{d} = \frac{2}{\pi} \left[ B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left( \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right) \right]$$

$$\text{where } A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} \left( 0.23 + \frac{0.11}{\epsilon_r} \right) \text{ and } B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}}$$

# Patch Antenna Dimensions for Inline-Feed - 1

## Calculation of patch<sup>11</sup>

We measure the width and  $\epsilon_{eff}$  of the patch using

$$W = \frac{1}{2f_0\sqrt{\mu_0\epsilon_0}}\sqrt{\frac{2}{\epsilon_r + 1}} \quad \epsilon_{eff} = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{\sqrt{1 + \frac{12h}{W}}}$$

Then, the length is measured as

$$\frac{\Delta L}{h} = 0.412 \frac{(\epsilon_{eff} + 0.3) \left(\frac{W}{h} + 0.264\right)}{(\epsilon_{eff} - 0.258) \left(\frac{W}{h} + 0.8\right)} \quad L_{eff} = \frac{c}{2f_0\sqrt{\epsilon_{eff}}}$$

and  $L = L_{eff} - 2\Delta L$

---

<sup>11</sup>All the calculations done using Python scripts

## Patch Antenna Dimensions for Inline-Feed - 2

### Calculation of Feed-point

We want to match antenna to

$$R_{in} = \frac{1}{2(G_1 \mp G_{12})} \cos^2 \left( \frac{\pi}{L} y_0 \right)$$

where  $l_1 = \int_0^\pi \frac{\sin^2 \left( \frac{k_0 W}{2} \cos \theta \right)}{\cos^2 \theta} \sin^3 \theta d\theta$  and  $G_1 = \frac{l_1}{120\pi^2}$

$$l_{12} = \int_0^\pi \frac{\sin^2 \left( \frac{k_0 W}{2} \cos \theta \right)}{\cos^e \theta} \sin^3 \theta \times \mathcal{J}_0(k_0 L \sin \theta) d\theta^{12} \text{ and}$$
$$G_{12} = \frac{l_{12}}{120\pi^2}$$

---

<sup>12</sup> $\mathcal{J}_0$  represents Bessel's function of 0 order

# Patch Antenna Dimensions for Inline-Feed - 3 and Dimensions for Resonators

## Constraints on the dimensions of the ground plane

- $\lambda_{eff} = \frac{c}{f_0} \sqrt{\epsilon_{eff}}$
- $L_{gnd} \geq L + 2 \times \frac{\lambda_{eff}}{4}$
- $W_{gnd} \geq W + 2 \times \frac{\lambda_{eff}}{4}$

## Dimension of resonators

The resonators are suppose to be quarter wavelength,  $L_r = \frac{\lambda}{4}$ , where  $\lambda$  is determined by  $f$  and  $\epsilon_{eff}^r$ <sup>13</sup>

---

<sup>13</sup>This is effective permittivity for resonator, which is different compared to that of the patch

