



# Designing Oscillator for an Antenna at $\sim 3.5$ GHz

2896

---

Mazz Shaikh(932056724), Nir Finch Cohen(230336612)

Edoh Shaulov

Tel Aviv University

## Milestones completed so far

---

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.

## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.



## List of Milestones completed

- Simulations evaluated a test schematic with an ideal transistor.
- LTSpice verified the design with the ideal transistor model.
- Selection of an RF transistor was based on simulation results.
- PSpice analyzed non-ideal behavior using the selected model.
- Essential data, like S-parameters, informed the matching network design.
- A matching network optimized impedance for  $Z_{out}$  and a  $50[\Omega]$  load at  $3.5[GHz]$ .
- Circuit power output was tested with the matching network, adjusting components for efficiency.



# Choosing the BJT

---

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## Required characteristics

- The transistor needs high-frequency performance, including  $f_{\max}$  and  $f_t$ , well above 3.5[GHz].
- Low parasitic capacitance at collector, base, and emitter terminals is crucial.
- Low noise figure is essential.
- High gain, especially at the operating frequency, is necessary for stable oscillation.
- Ensure appropriate biasing for Colpitts oscillator operation, including DC voltages and currents.

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)



## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|$ ,  $G_{ma}$ ,  $G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)

## BFP520 from Infineon<sup>1</sup>

- Surface mount low voltage silicon NPN RF bipolar transistor
- Transition frequency  $f_T$  of 45[GHz]
- High Gain, with  $|S_{12}|, G_{ma}, G_{ms} > 16[dB]$  at 3.5[GHz] under  $V_{ce} = 2[V]$
- Low Noise Figure,  $NF < 1.2[dB]$  at 3.5[GHz], 2[V], 2[mA]

---

<sup>1</sup>[https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02\\_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a](https://www.infineon.com/dgdl/Infineon-BFP520-DS-v02_00-EN.pdf?fileId=5546d462689a790c01690f035fe2391a)



# Oscillator Circuit

---


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

<sup>a</sup>

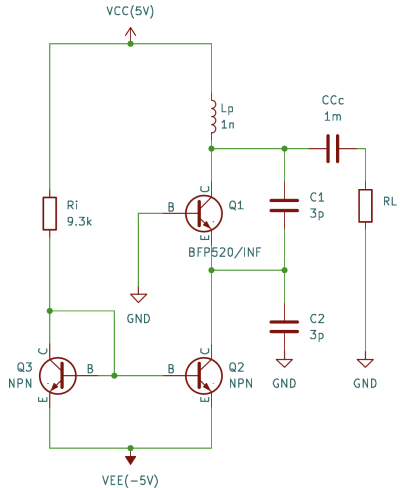- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

a

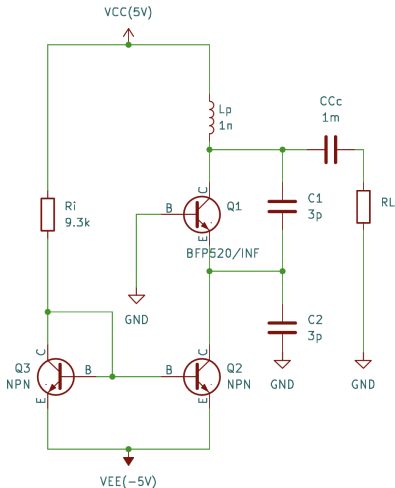- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix


# Collpit's Oscillator

- The circuit was tested with some high impedance load attached
- Values of  $L_p$ ,  $C_1$  and  $C_2$  were computed using the operating frequency formula

$$f_c \approx \frac{1}{2\pi \sqrt{L_p \frac{C_1 C_2}{C_1 + C_2}}}$$

<sup>a</sup>

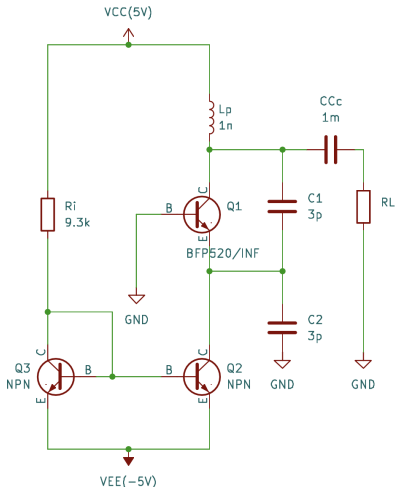- $C_1 = C_2$  was chosen since it gave the highest oscillation frequency



<sup>a</sup>In-depth analysis in Appendix



# Output Waveform




# Choosing a Matching Network

---
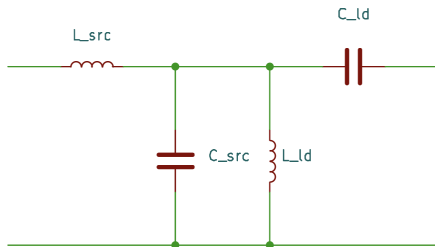
# Matching Network

T-matching is better for matching a load to a source impedance when there's a large disparity because it provides efficient power transfer, minimizes losses, and offers impedance transformation with stability.<sup>2</sup>

- $L_{src} =$
- $C_{src} =$
- $L_{ld} =$
- $C_{ld} =$



---

<sup>2</sup>Design method in Appendix

## S-parameters of the Matching Network

Tested with  $R_S = 1000[\Omega]$  and  $R_L = 50[\Omega]$

## Output of Oscillator using Matching Network as $50[\Omega]$ load



# Efficiency $\eta$

---

## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}^3$

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$ <sup>3</sup>

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%



## Defining $\eta$

- **Input:**  $P_{DC} = V_{CC}I_C$
- **Output:**  $P_{ac} = \frac{V_{rms}^2}{R_L}$  where  $V_{rms} = \frac{V_{max}}{\sqrt{2}}$  for the output waveform
- **Efficiency:**  $\eta = \frac{P_{ac}}{P_{CD}}$ <sup>3</sup>

---

<sup>3</sup>It has been shown (Krauss, et al., 1980) that the maximum theoretical efficiency for this oscillator configuration is 25%

## Calculation of $\eta$



## Next Steps

---

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps

- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

## Next Steps



- Create an antenna at 3.5[GHz]
- Measure S-parameters of the antenna and of the whole system
- Layout the PCB
- Fabrication and Testing

# Appendix



---



# Data from Infenion - 1

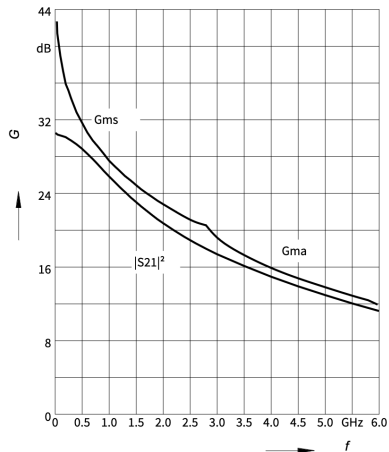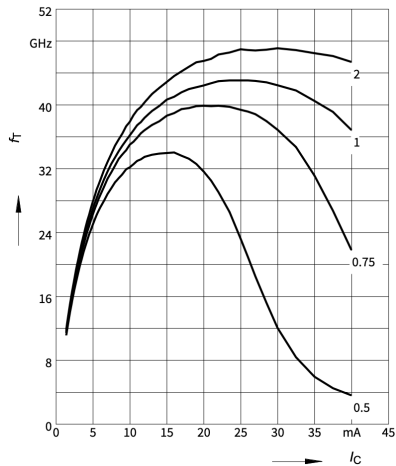

## Data from Infenion - 2

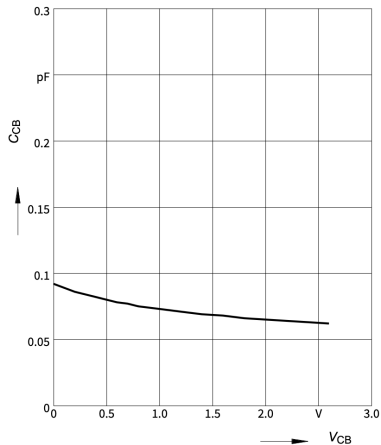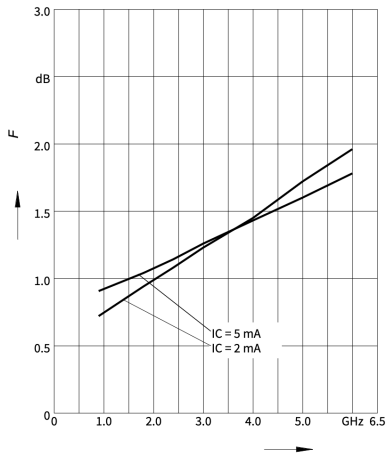

# BFP520 Spice File


```
*$
.SUBCKT BFP520/INF 200 100 300
L1 1 10 0.47nH
L2 2 20 0.56nH
L3 3 30 0.23nH
C1 10 20 6.9fF
C2 20 30 134fF
C3 30 10 136fF
L4 10 100 0.53nH
L5 20 200 0.58nH
L6 30 300 0.05nH
Q1 2 1 3 BFP520
.ENDS
.MODEL BFP520 NPN(
+ IS =1.5E-17 NF =1 NR =1
+ ISE=2.5E-14 NE =2 ISC=2E-14
+ NC =2 BF =235 BR =1.5
+ VAF=25 VAR=2 IKF=0.4
+ IKR=0.01 RB =11 RBM=7.5
+ RE =0.6 RC =7.6 CJE=2.35E-13
+ VJE=0.958 MJE=0.335 CJC=9.3E-14
+ VJC=0.661 MJC=0.236 CJS=0
+ VJS=0.75 MJS=0.333 FC=0.5
+ XCJC=1 TF=1.7E-12 TR=5E-08
+ XTF=10 ITF=0.7 VTF=5
+ PTF=50 XTB=-0.25 XTI=0.035
+ EG=1.11)
```

\*\*\*\*\*

\*\$
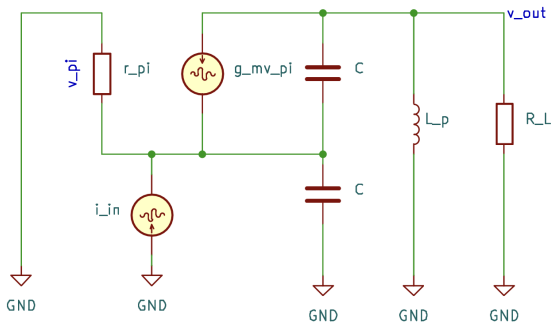
# Proof of operating frequency - 1

We have the following small signal model of Collpit's oscillator, with  $C_1 = C_2 = C^4$



---

<sup>4</sup>In all the results, we try to ignore effects of  $r_{\pi}$  and then adjust the values accordingly to get required response

## Proof of operating frequency - 2

$$i_{in} = -\frac{v_{\pi}}{r_{\pi}} - sC(v_{out} + 2v_{\pi})$$

$$g_m v_{\pi} + sC(v_{out} + v_{\pi}) + \frac{v_{out}}{sL_p} + \frac{v_{out}}{R_L} = 0$$

This gives us the following frequency response

$$\frac{v_{out}}{i_{in}} = \frac{r_{\pi} L_p R_L (s^2 C + s g_m)}{r_{\pi} C^2 L_p R_L s^3 + (-r_{\pi} C L_p R_L g_m + 2r_{\pi} C L_p + C L_p R_L) s^2 + (2r_{\pi} C R_L + L_p) s + R_L}$$

Put  $s = j\omega$  and let  $Im$  of denominator  $\rightarrow 0$

$$\omega_0 = \sqrt{\frac{2r_{\pi} C R_L + L_p}{r_{\pi} C^2 L_p R_L}}$$

Assuming  $r_{\pi} \rightarrow \infty$ , as is the case is MOS, we reach the well-known expression  $\omega_0 = \sqrt{L \frac{1}{C \cdot C}}$

## Proof of operating frequency - 3

For sustained oscillations, we need

$$-(r_{\pi}CL_pR_Lg_m + 2r_{\pi}CL_p + CL_pR_L)\omega_0^2 + R_L > 0$$

This gives us

$${}^5R_Lg_m - \frac{R_L}{r_{\pi}} - 2 > 0$$

Thus, we need to set  $R_L$  accordingly at the oscillating frequency, giving us a lower bound for load and thus a need for a matching network.

---

<sup>5</sup>This is similar to the condition found in Razavi, but for NMOS in place of NPN BJT

# Calculation of matching network - 1

We have a source impedance  $Z_s$ , a load impedance  $Z_L$ , and operating frequency  $f_0$  and we need to match  $Z_L$  to  $Z_s$  at  $f_0$  using a T-Matching Network. We assume a central impedance  $Z_c$  such that  $Z_c > \max(Z_s, Z_L)$ , and then calculate the series and parallel reactive components on both sides.<sup>6</sup>

Source:

$$Q_{src} = \sqrt{\frac{Z_c}{Z_s} - 1}$$

$$X_{src}^{parallel} = \frac{Z_c}{Q_{src}}$$

$$X_{src}^{series} = Q_{src} Z_s$$

Load:

$$Q_{ld} = \sqrt{\frac{Z_c}{Z_L} - 1}$$

$$X_{ld}^{parallel} = \frac{Z_c}{Q_{ld}}$$

$$X_{ld}^{series} = Q_{ld} Z_L$$

Then,  $L = \frac{X}{2\pi f_0}$  and  $C = \frac{1}{2\pi f_0 X}$  for chosen  $X$  series/parallel

---

<sup>6</sup>In our case, all impedances are real

## Calculation of matching network - 2

Variable	Value
$f_0$	$3.5 \times 10^9$
$Z_{\text{out\_osc}}$	1000
$Z_{\text{load}}$	50
$Z_{\text{center}}$	1002
$Q_{\text{src}}$	0.0447214
$X_{\text{paralle\_src}}$	22405.4
$X_{\text{series\_src}}$	44.7214
$L_{\text{src}}$	$2.03361 \times 10^{-9}$

Variable	Value
$C_{\text{src}}$	$2.02955 \times 10^{-15}$
$Q_{\text{ld}}$	4.36348
$X_{\text{paralle\_ld}}$	229.633
$X_{\text{series\_ld}}$	218.174
$L_{\text{ld}}$	$1.04421 \times 10^{-8}$
$C_{\text{ld}}$	$2.08424 \times 10^{-13}$
$C_{\text{com}}$	$2.10454 \times 10^{-13}$
$L_{\text{com}}$	$1.70212 \times 10^{-9}$